

Continuous Assessment Test (CAT) - I - FEB 2024

Programme	3.4	B.Tech. (ECE)	Semester: Winter 2023-24
Course Code & Course Title		BECE302L & Control Systems	Class Number: CH2023240501029 CH2023240500989 CH2023240500984
Faculty	:	Dr. M. Jagannath Dr. Sunil Kumar Pradhan Dr. Ashis Tripathy	Slot: F1+TF1
Duration	:	90 Minutes	Max. Mark: 50

General Instructions:

- Write only your registration number on the question paper in the box provided and do not write other information.
- Use statistical tables supplied from the exam cell as necessary.
- Use graph sheets supplied from the exam cell as necessary.
- Only non-programmable calculator without storage is permitted.

Answer all questions

Q. No	Sub Sec.	Description	Marks
ð	(a)	Give any two real-time examples of open-loop and closed-loop control systems and derive the transfer function of a negative feedback system.	
	(b)	Determine the transfer function from Figure 1. C_1 R_1 R_2 R_2 R_2 R_2 R_2 R_3 R_4 R_2 R_4 R_4 R_5 R_5 R_6 R_7 R_8 R_9 R	5
		Figure 1.	
2		Write the differential equations governing the electrical circuit as shown in Figure 2.	5
		Figure 2.	

